
CMPEN 411

VLSI Digital Circuits

Spring 2012

Lecture 21: Shifters, Decoders, Muxes

[Adapted from Rabaey's *Digital Integrated Circuits*, Second Edition, ©2003
J. Rabaey, A. Chandrakasan, B. Nikolic]

Review: Basic Building Blocks

❑ Datapath

- Execution units
 - Adder, multiplier, divider, **shifter**, etc.
- Register file and pipeline registers
- **Multiplexers, decoders**

❑ Control

- Finite state machines (PLA, ROM, random logic)


❑ Interconnect

- Switches, arbiters, buses

❑ Memory

- Caches (SRAMs), TLBs, DRAMs, buffers


Parallel Programmable Shifters

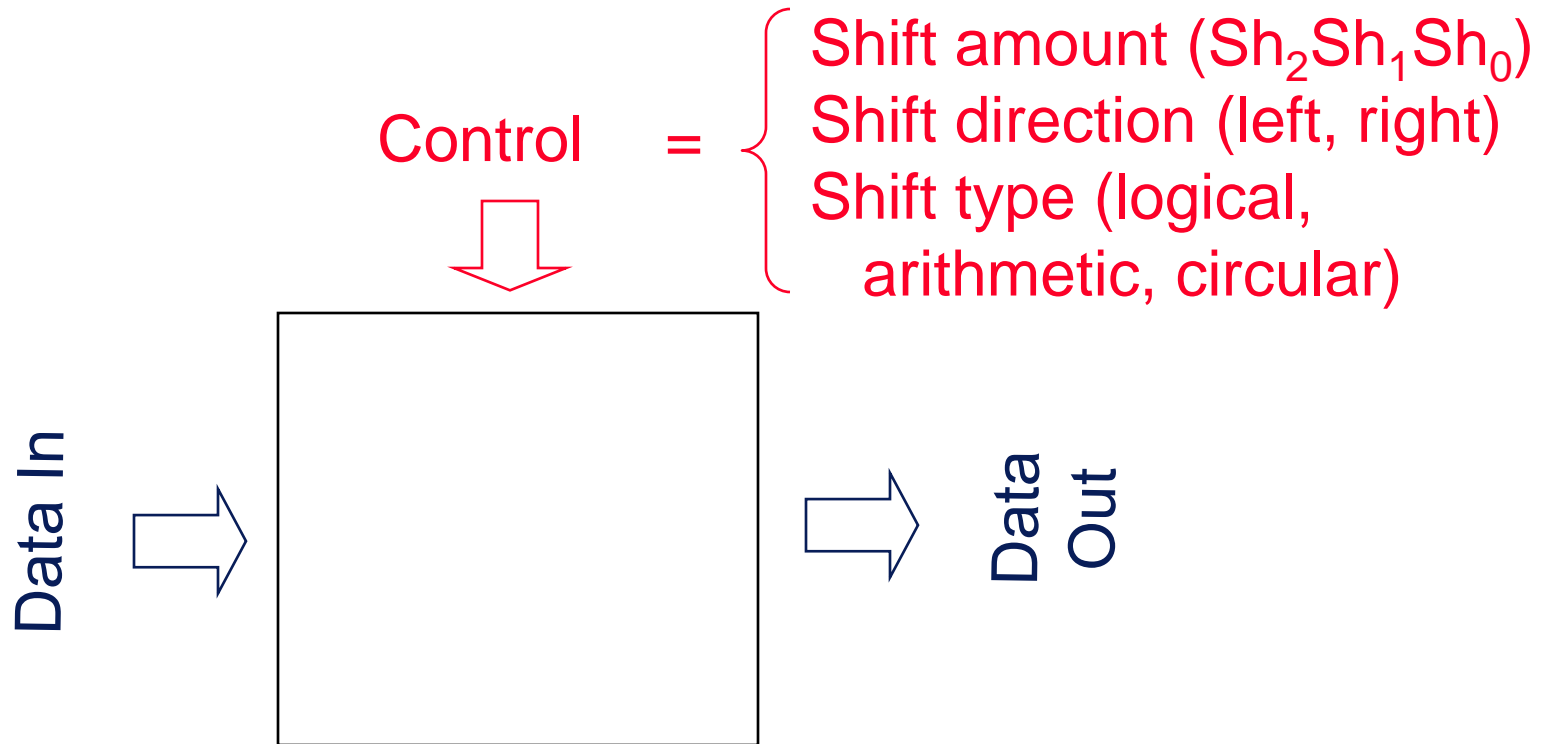

Shifters used in multipliers, floating point units


Consume lots of area if done in random logic gates

A Programmable Binary Shifter

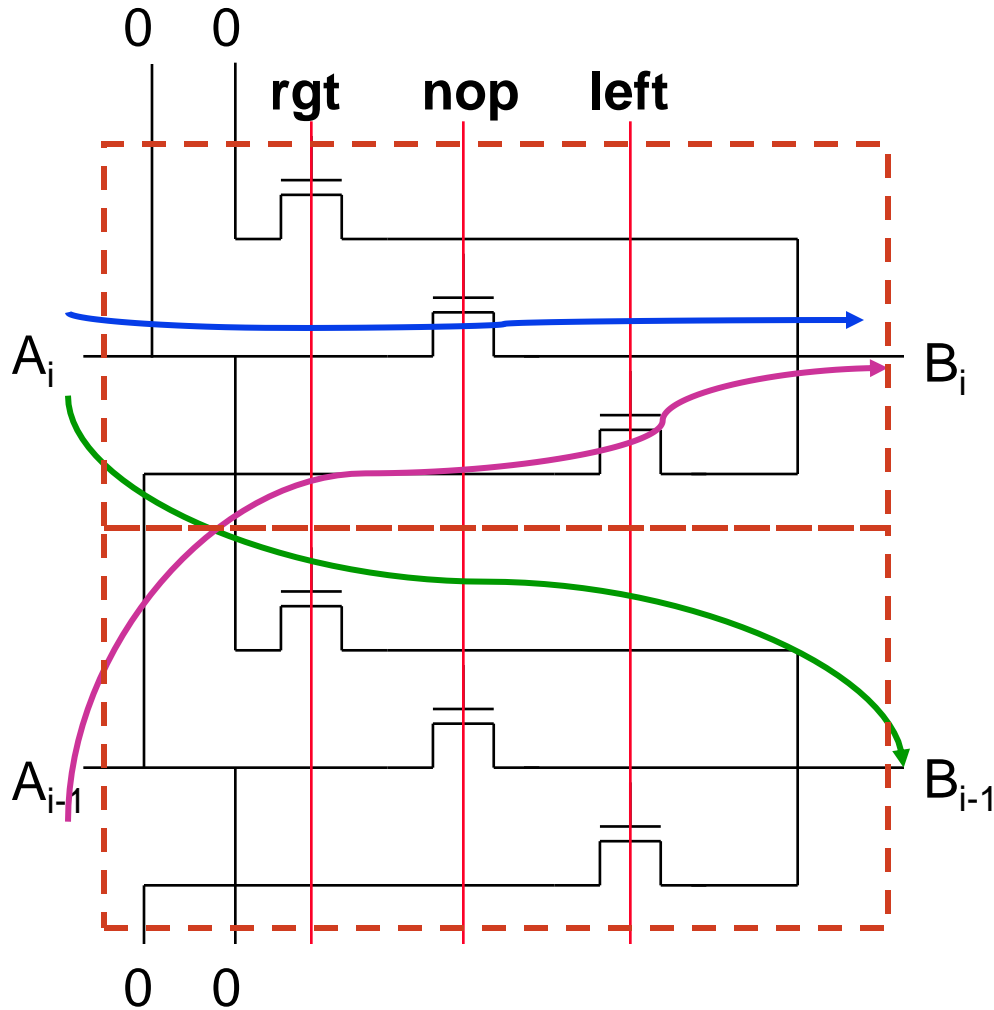

A_i	A_{i-1}	rgt	nop	left	B_i	B_{i-1}
A_1	A_0	0	1	0	A_1	A_0
A_1	A_0	1	0	0	0	A_1
A_1	A_0	0	0	1	A_0	0

4-bit Barrel Shifter

 

Example:

$$!Sh_1!Sh_0 = 1$$

$$B_3B_2B_1B_0 = A_3A_2A_1A_0$$

$$!Sh_1Sh_0 = 1$$

$$B_3B_2B_1B_0 = A_3A_3A_2A_1$$

$$Sh_1!Sh_0 = 1$$


$$B_3B_2B_1B_0 = A_3A_3A_3A_2$$

$$Sh_1Sh_0 = 1$$

$$B_3B_2B_1B_0 = A_3A_3A_3A_3$$

Area dominated by wiring

4-bit Barrel Shifter Layout

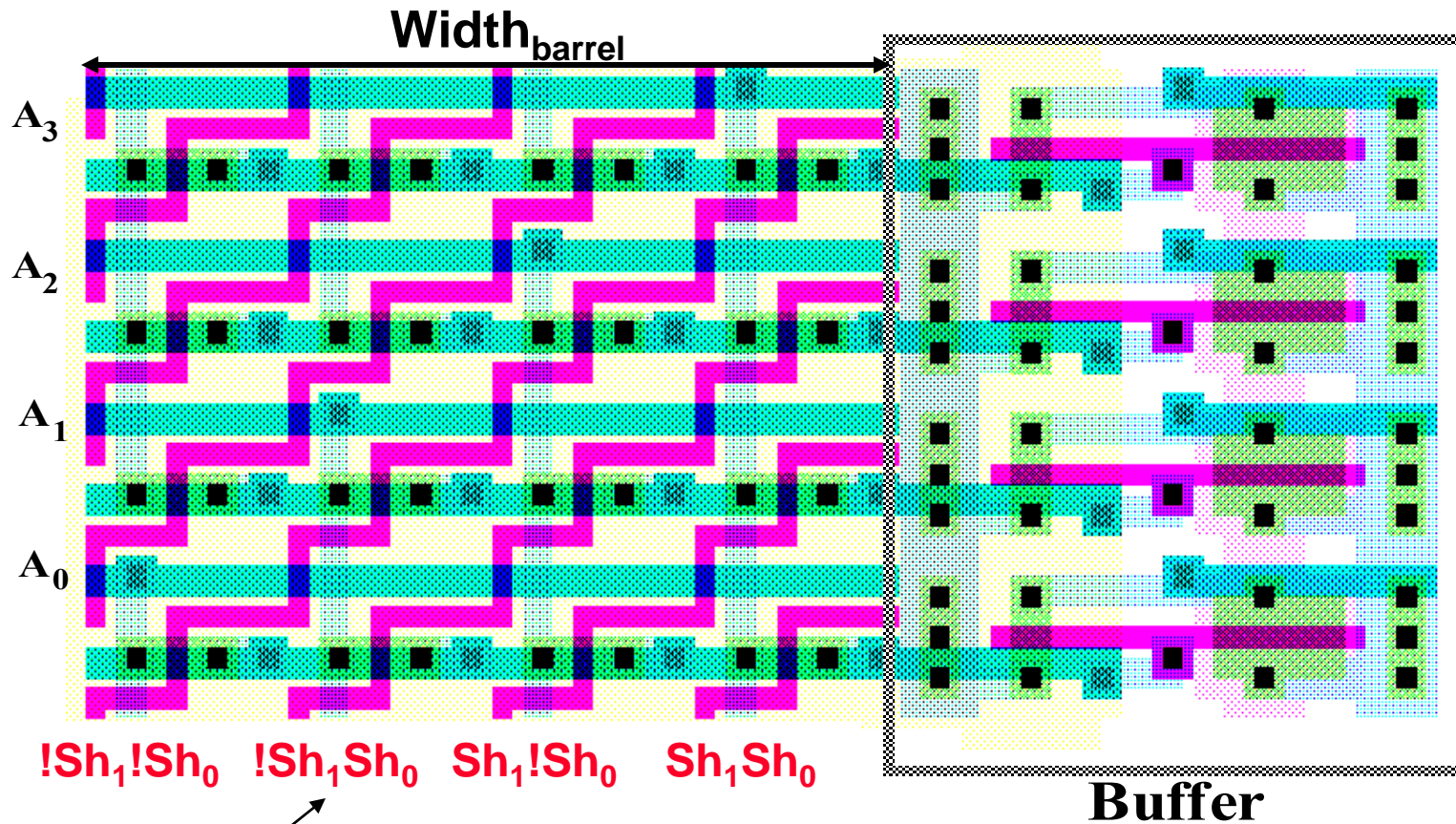


Only one Sh#
active at a time_i


Width_{barrel} ~ O(N)

Delay ~ 1 fet + N diff caps


Logarithmic Shifter Structure

 

8-bit Logarithmic Shifter

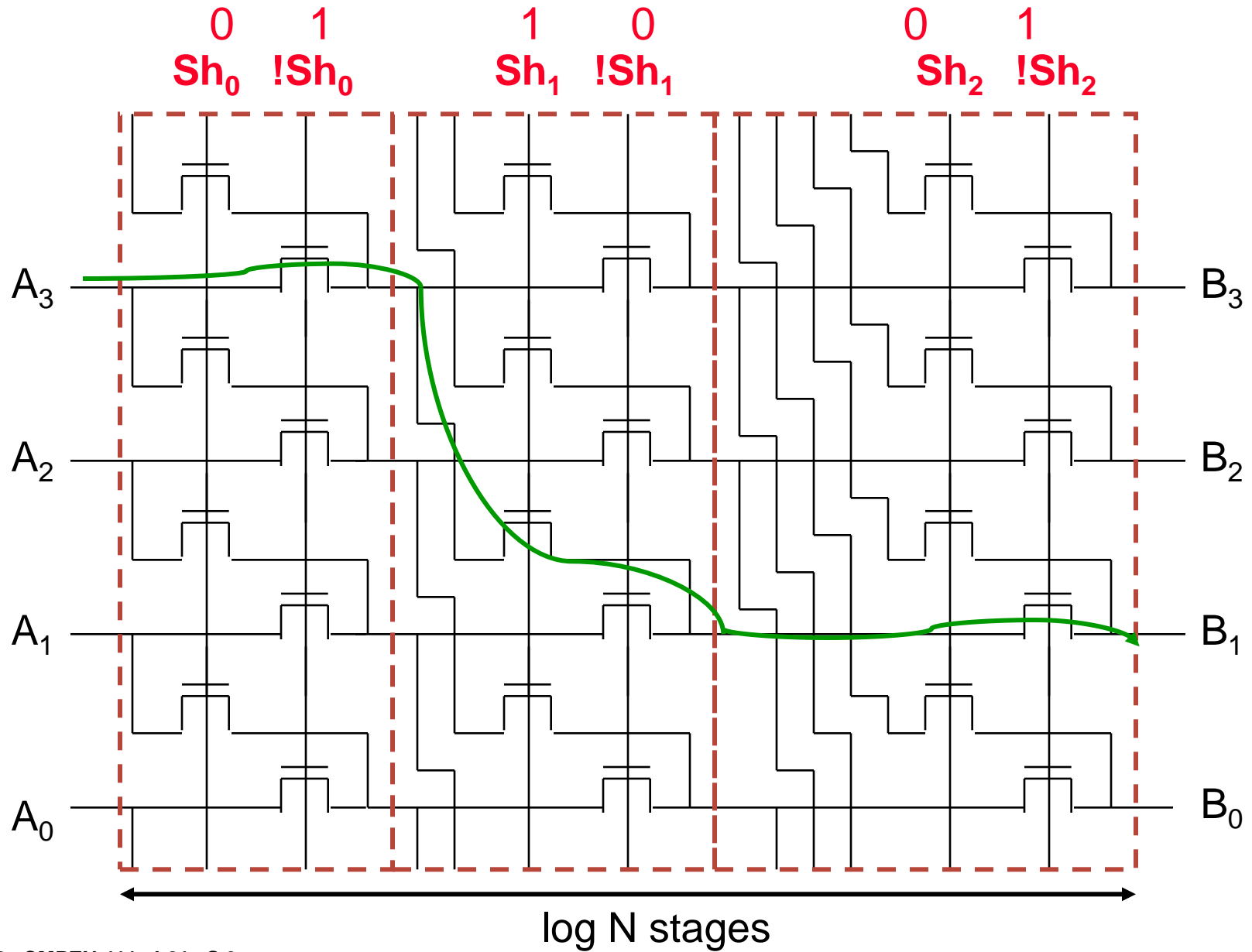

8-bit Logarithmic Shifter Layout Slice

 

$K = \log_2 N$
Delay $\sim K$ fets + 2 diff caps


Shifter Implementation Comparisons

N	K	Barrel		Logarithmic	
		Width	Speed	Width	Speed
		$2 N p_m$	$1 + N$ diffs	$p_m(2^K+2K-1)$	$K + 2$ diffs
8	3	$16 p_m$	$1 + 8$	$13 p_m$	$3 + 2$
16	4	$32 p_m$	$1 + 16$	$23 p_m$	$4 + 2$
32	5	$64 p_m$	$1 + 32$	$41 p_m$	$5 + 2$
64	6	$128 p_m$	$1 + 64$	$75 p_m$	$6 + 2$

Barrel shifter needs an $K \times 2^K$ shift amount decoder


Decoders

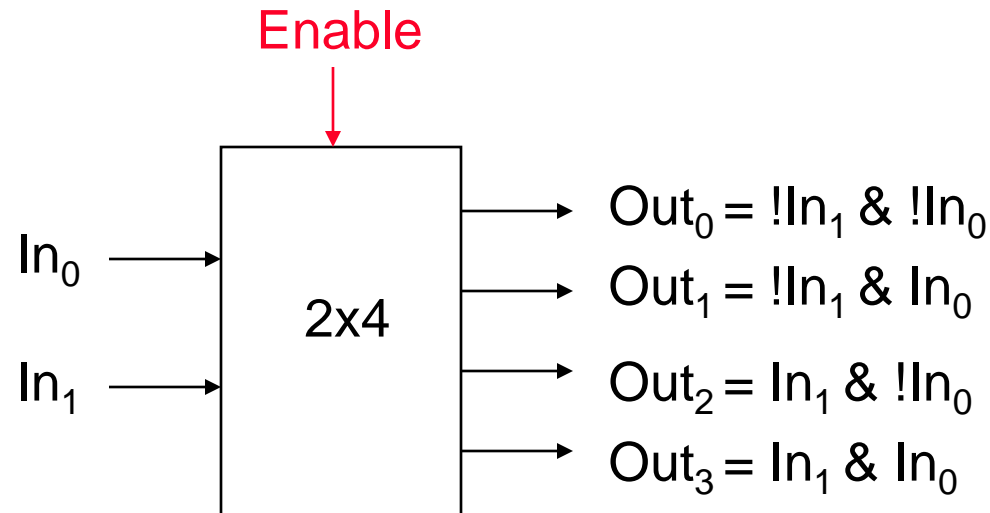- ❑ Decodes inputs to activate one of many outputs




- In random gate logic need two inverters, four 2-input nand gates, four inverters plus enable logic
- how about for a 3-to-8, 4-to-16, etc. decoder?

Dynamic NOR Row Decoder

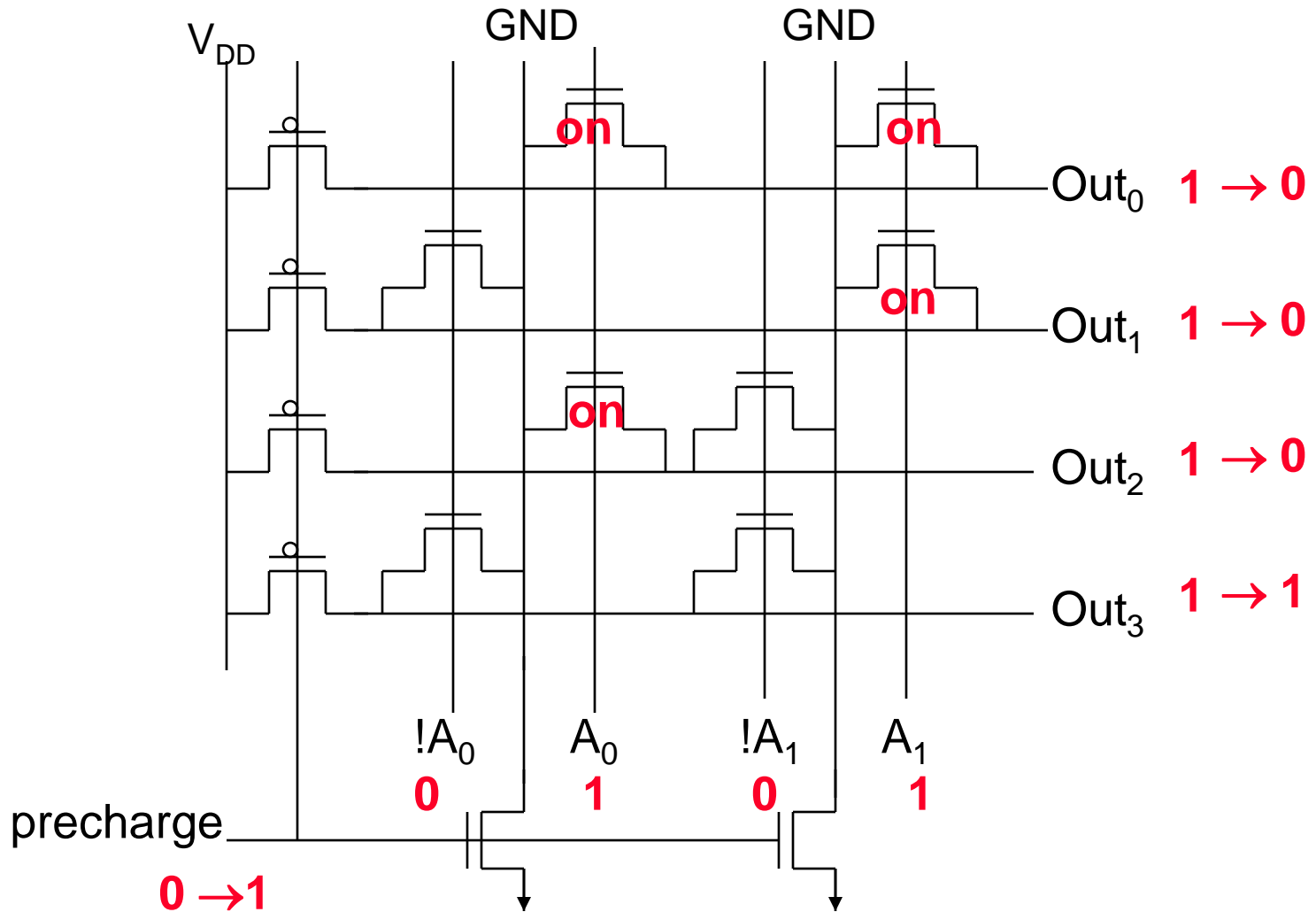


Dynamic NAND Row Decoder

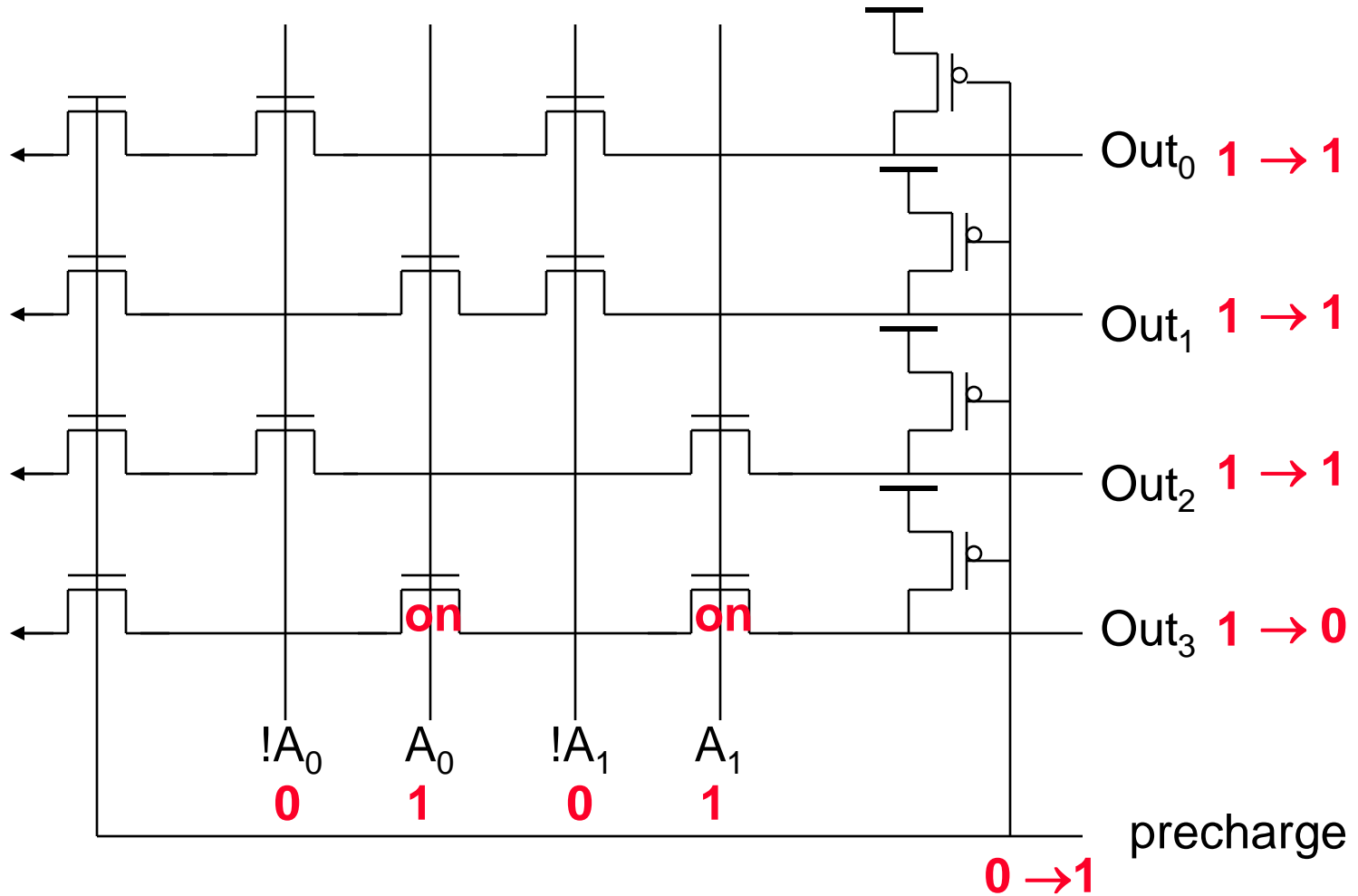


Building Big Decoders from Small

Active low enable
Active low output

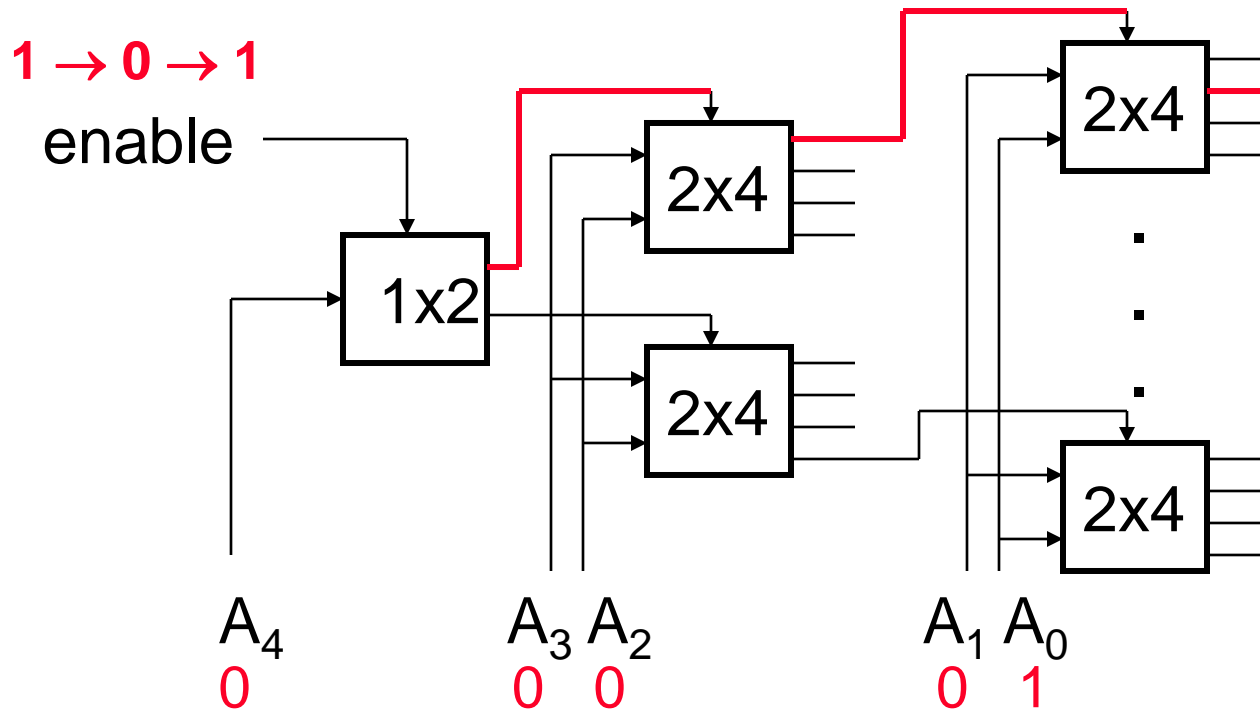


Multiplexers

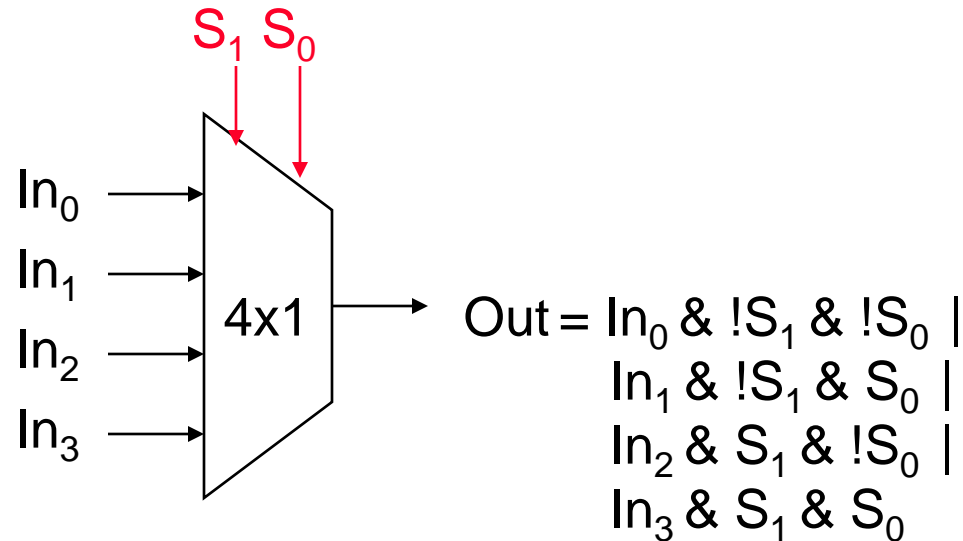- ❑ Selects one of several inputs to gate to the single output




- In random gate logic need two inverters, four 3-input nands, one 4-input nand
- how about for an 8x1, 16x1, etc. mux?


Review: TG 2x1 Multiplexer

 

$$F = !((In_1 \& S) | (In_2 \& !S))$$

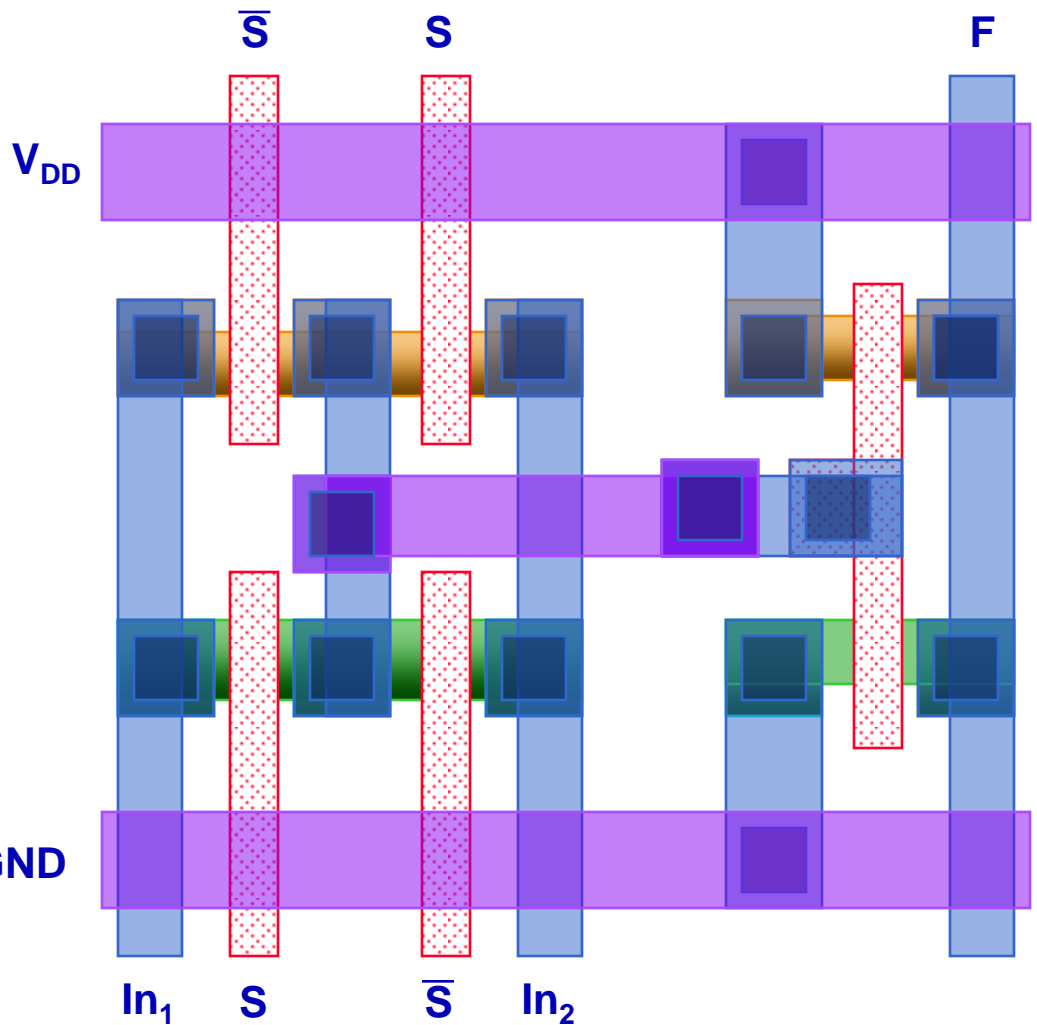

Building Big Muxes from Small

 

Next Lecture and Reminders

□ Next lecture

- SRAM, DRAM, and CAM cores
 - Reading assignment – Rabaey, et al, 12.1-12.2.4