
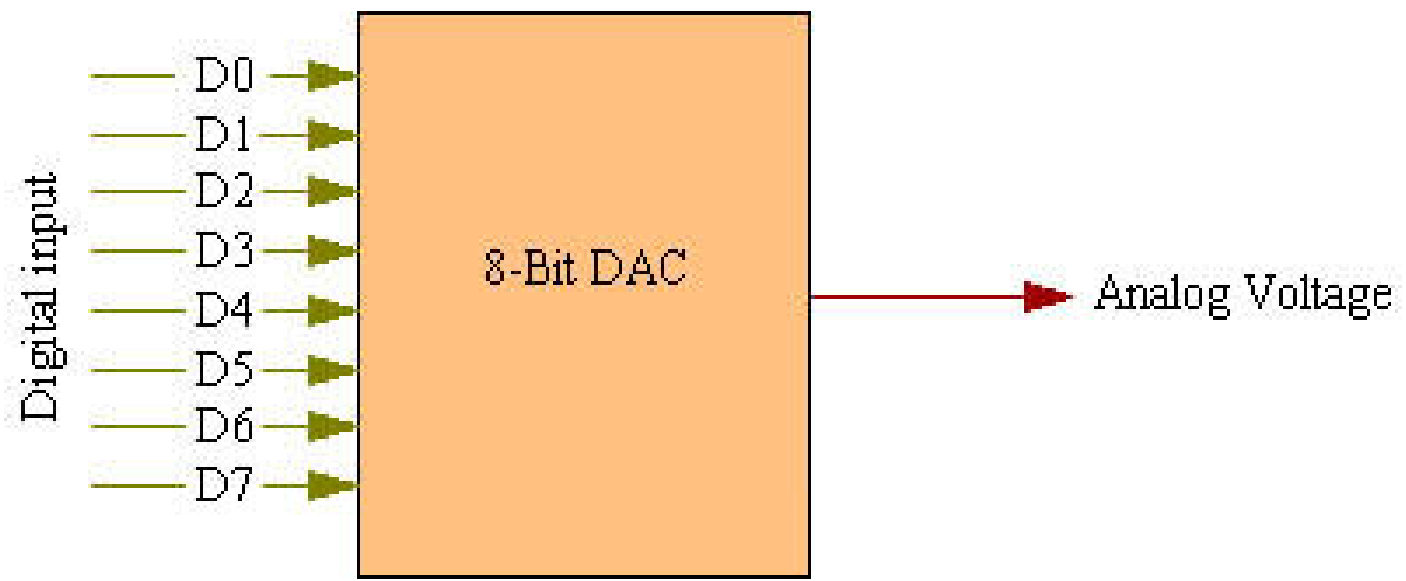


Digital to Analog Converter

 


Pulse Width Modulation (PWM)





$$\text{Duty cycle} = t_2 / t_1$$

Pulse Width Modulation (PWM)

 


$$\text{Duty cycle} = t_2 / t_1$$

 
 


Output: smooth DC


Pulse Width Modulation (PWM)

 

Pulse Width Modulation (PWM)

  

Resistor String DAC

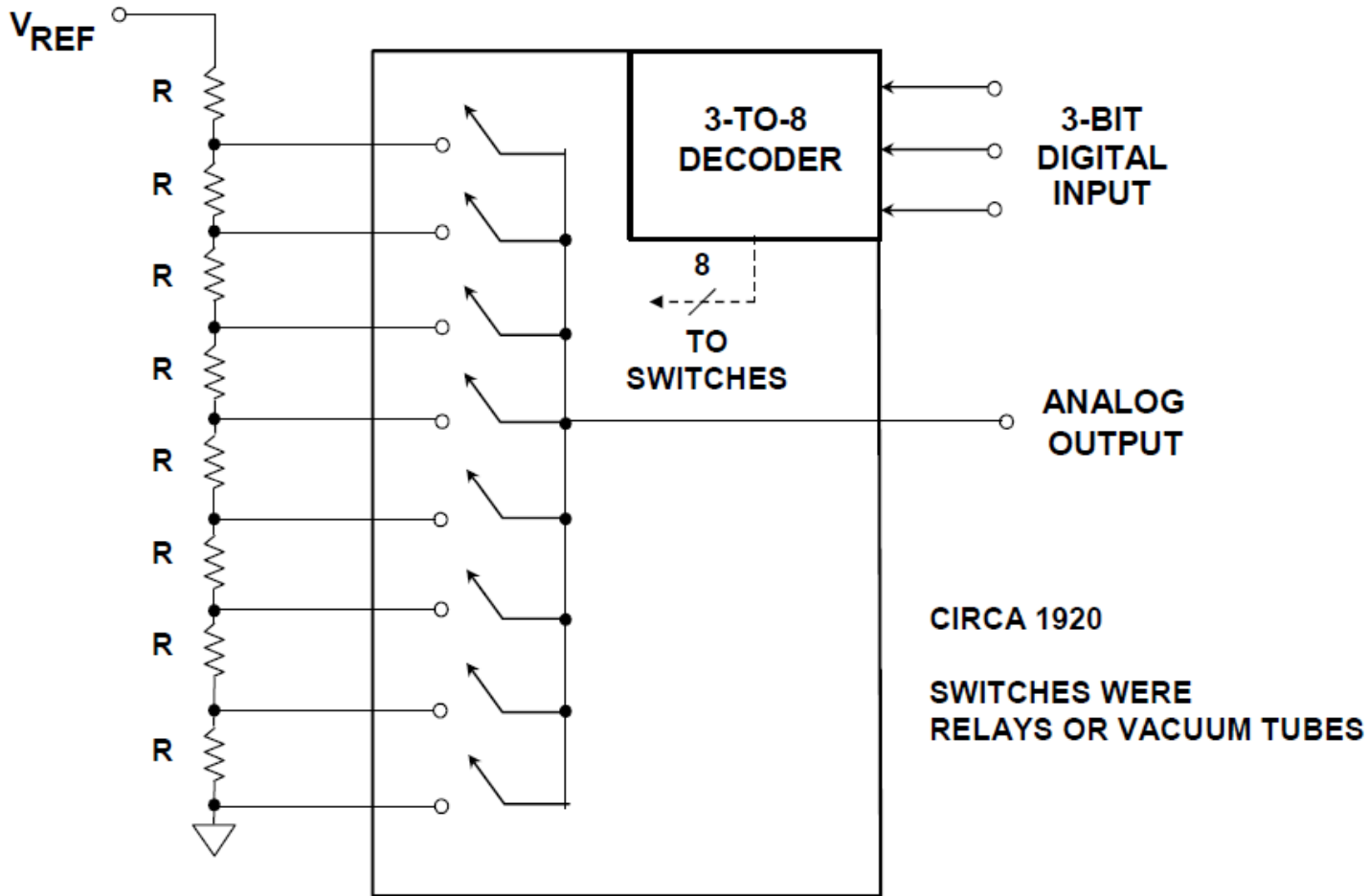

**Figure 2: Simplest Voltage-Output Thermometer DAC:
The Kelvin Divider ("String DAC")**

Resistor String DAC

 


Figure 4: The Simplest Current-Output Thermometer (Fully-Decoded) DAC

Resistor String DAC

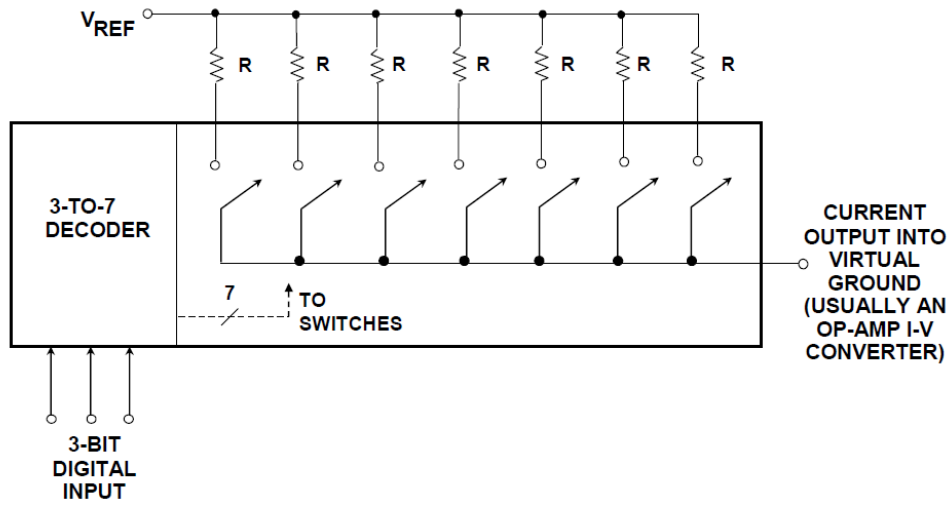


Figure 4: The Simplest Current-Output Thermometer (Fully-Decoded) DAC

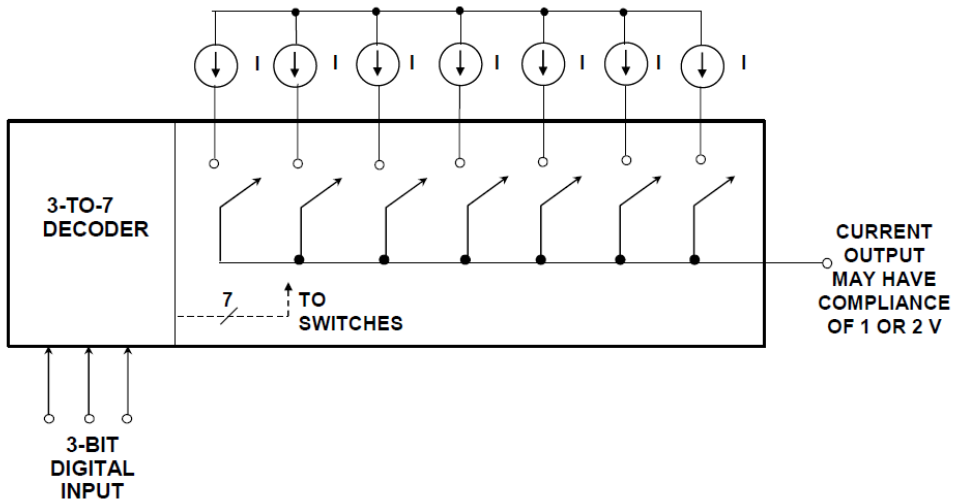


Figure 5: Current Sources Improve the Basic Current-Output Thermometer DAC

Resistor String DAC

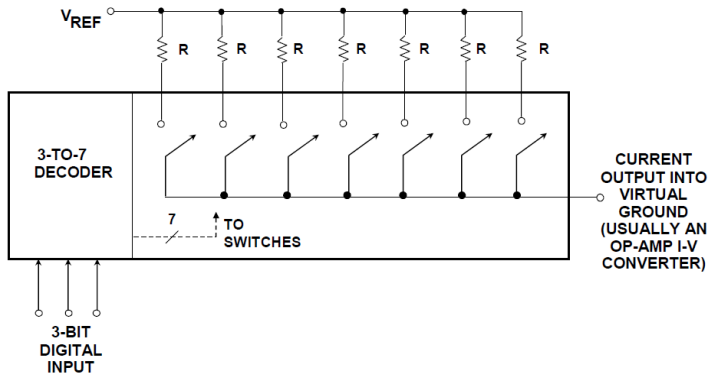


Figure 4: The Simplest Current-Output Thermometer (Fully-Decoded) DAC

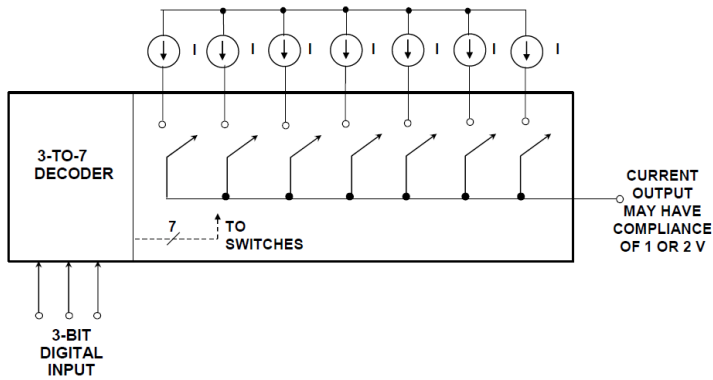


Figure 5: Current Sources Improve the Basic Current-Output Thermometer DAC

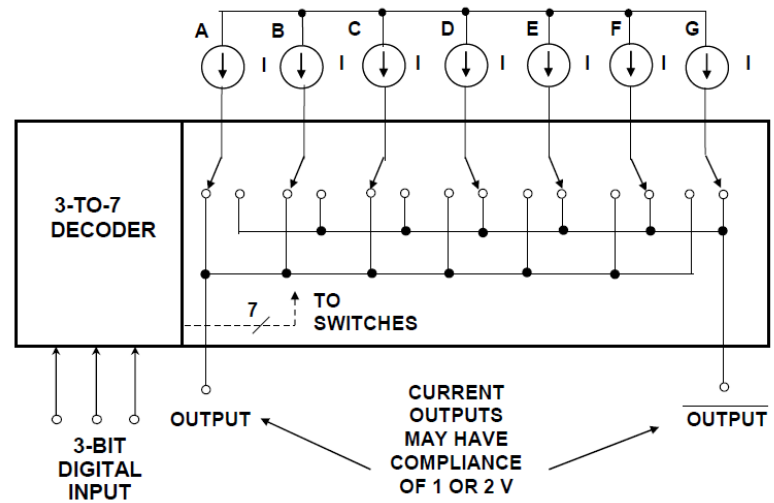


Figure 6: High Speed Thermometer DAC with Complementary Current Outputs

Resistor String DAC

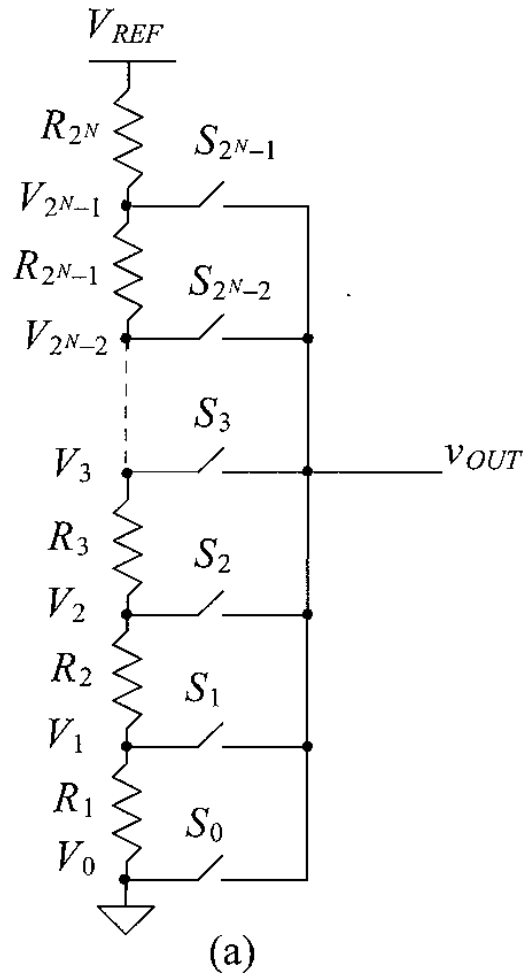


Figure 29.2 (a) A simple resistor-string DAC.

Resistor String DAC



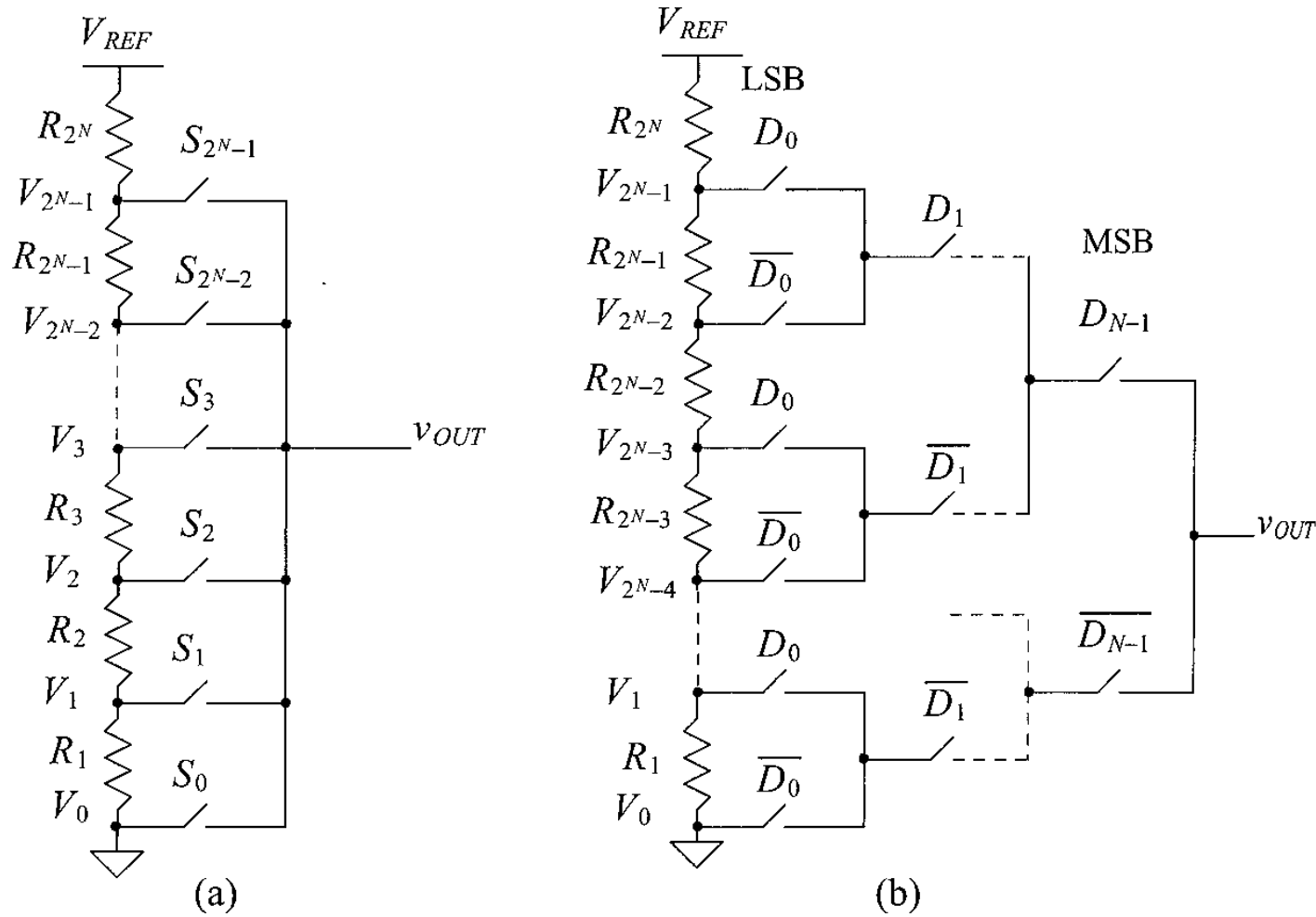


Figure 29.2 (a) A simple resistor-string DAC and (b) the use of a binary switch array to lower the output capacitance.

Inverting Op Amp

 


Inverting summer circuit

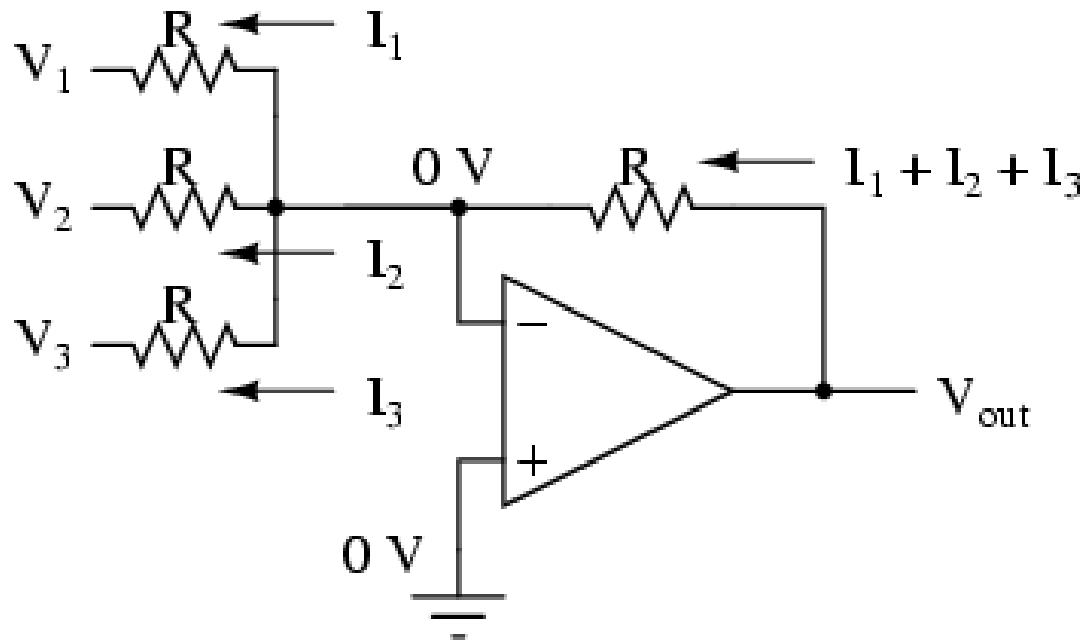


$V_{\text{out}} =$

Inverting summer circuit

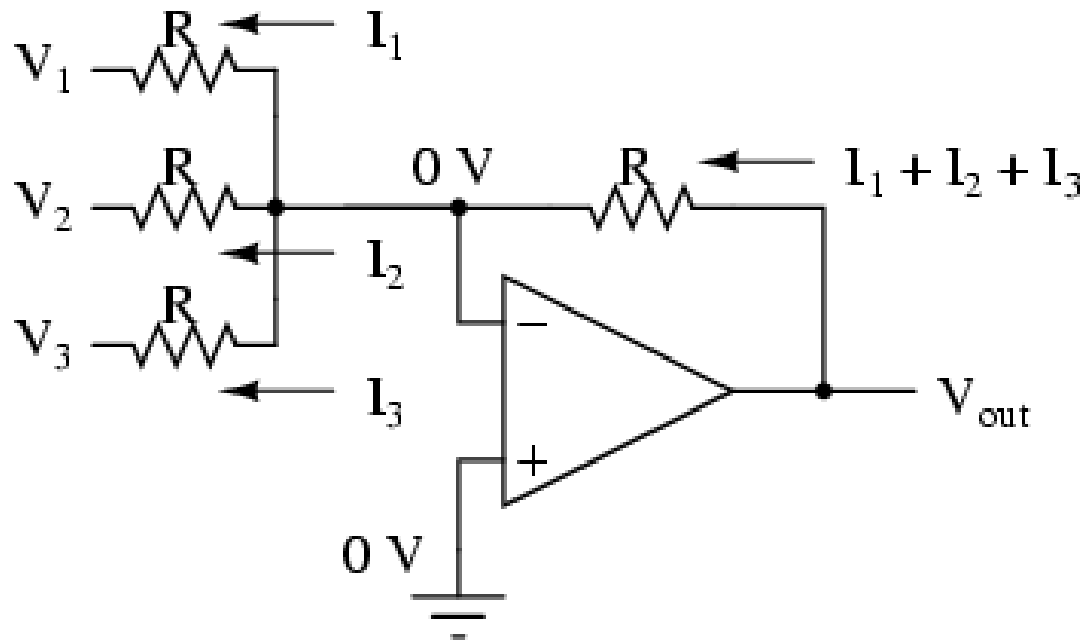


$$V_{\text{out}} = - (V_1 + V_2 + V_3)$$

DAC with Weighted Sum

 


$$V_{out} = - \left(V_1 + \frac{V_2}{2} + \frac{V_3}{4} \right)$$


6-bit binary-weighted DAC

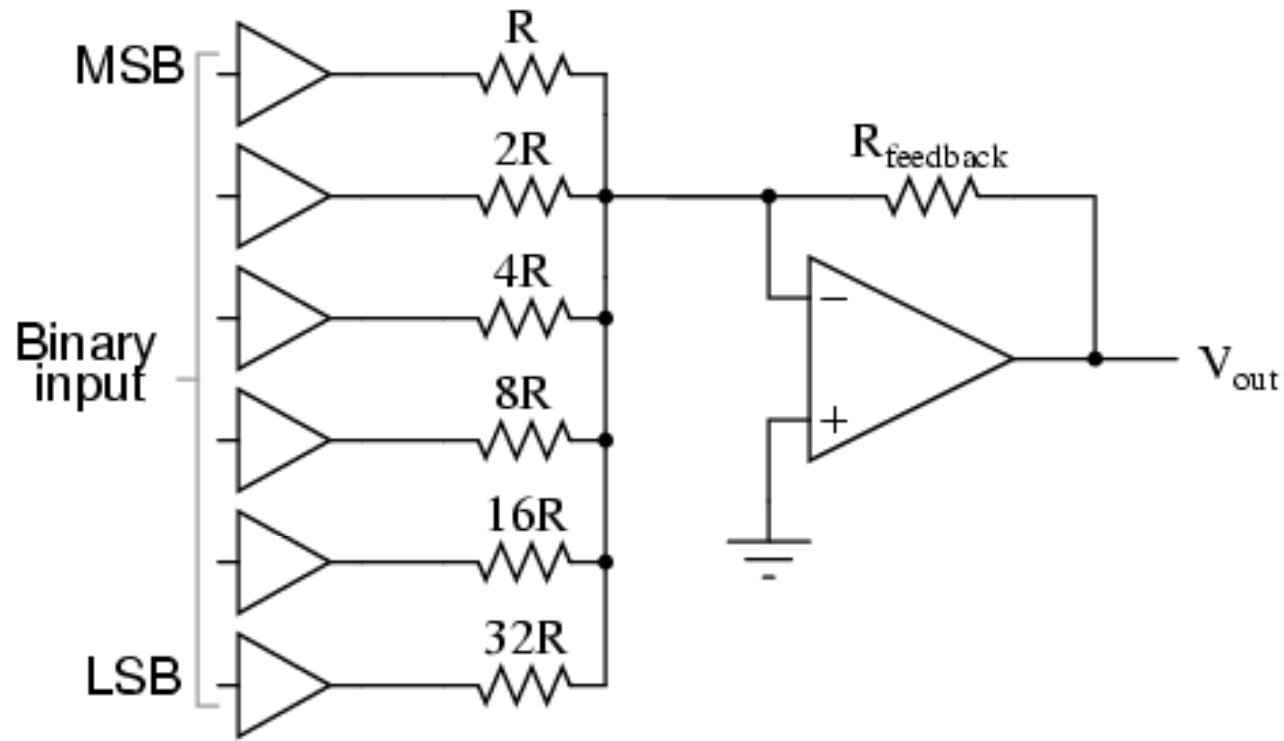


Binary Weighted DAC

 



Binary Weighted DAC


 


R/2R "ladder" DAC

 

 

 

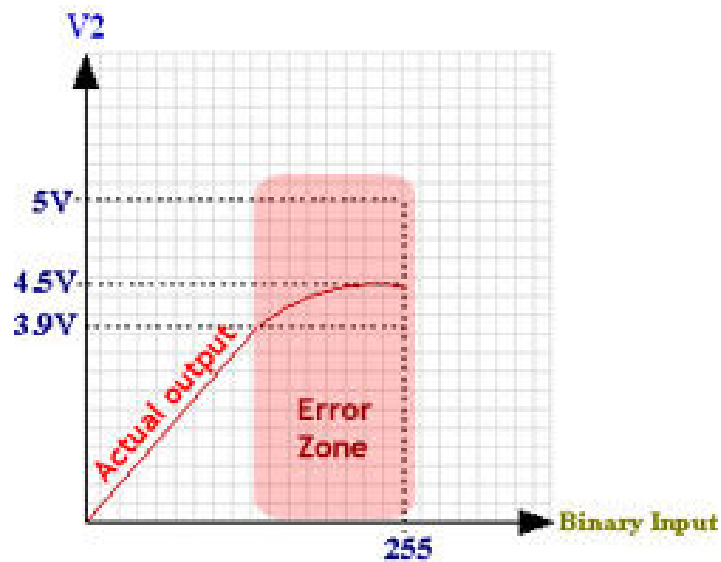 


8 BIT R/2R DAC performance
www.ikalogic.com

DAC Implementation

Table 30.1 Summary of experimental results.

	8-bit	10-bit	12-bit
DNL (LSB)	0.150	0.450	2.000
INL (LSB)	0.200	1.000	3.000
Settling time	200 ns		
Power	3.88 mW (driving a 1k load)		
Area (mm ²)	0.045		
$f_{clk,max}$	4 MHz		
Output swing	$0 < V_{out} < VDD (= 1.8 V)$		

 

DAC Implementation

 


Figure 30.4 Experimental results for the wide-swing DAC of Fig. 30.3.

Pipeline DAC

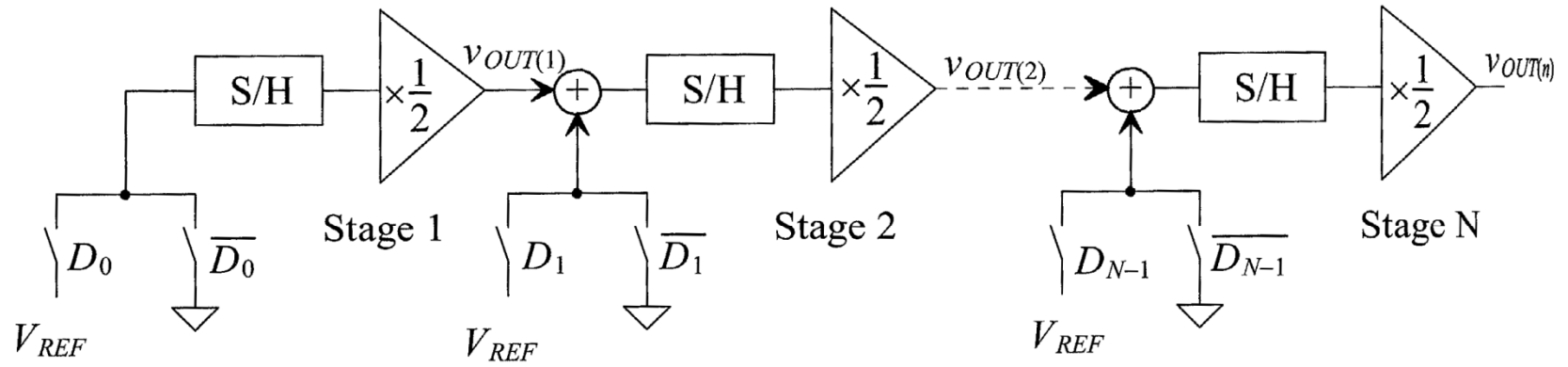


Figure 29.19 A pipeline digital-to-analog converter.

Digital to Analog Converter